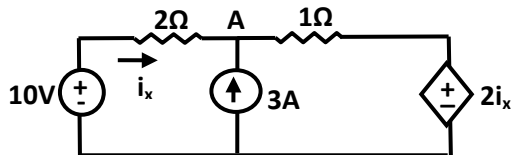


Answer Keys: ECE-TS-1

1	C	2	A	3	B	4	C	5	C	6	B	7	A	8	B	9	B	10	B
11	D	12	B	13	B	14	B	15	A	16	B	17	C	18	D	19	A	20	C
21	B	22	D	23	B	24	C	25	A	26	A	27	B	28	B	29	C	30	C
31	C	32	C	33	A	34	A	35	D	36	C	37	D	38	B	39	D	40	C
41	D	42	B	43	A	44	C	45	B	46	B	47	A	48	B	49	C	50	D
51	C	52	C	53	C	54	B	55	B	56	D	57	A	58	C	59	A	60	B
61	C	62	B	63	B	64	D	65	C										

Explanation:

1. [Ans .C], Applying KCL at node A; and node voltage



$$i_x + 3 = \frac{v - 2i_x}{1} \text{ ----- (1)}$$

$$i_x = \frac{10 - v}{2} \text{ ----- (2)}$$

$$\Rightarrow v = -2i_x + 10$$

Replacing in 1,


$$i_x + 3 = -2i_x + 10 - 2i_x$$

$$\Rightarrow 5i_x = 7$$

$$\Rightarrow i_x = 7/5 = 1.4A,$$

Option (C) is correct

2. [Ans .A],

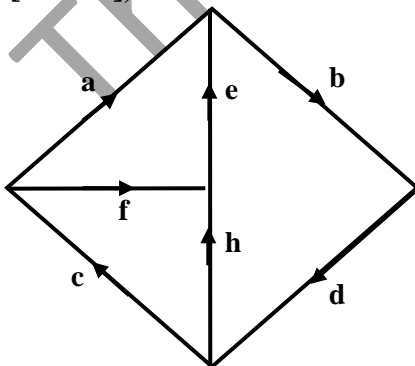

Option (A): e f g h, since current sources are O.C in a graph.

3. [Ans .B], $\frac{d(V_L - V_C)}{dI_L} = \frac{dV_R}{dI_L} (\because V_R(t) = V_L(t) - V_C(t))$
 $= \frac{-dV_R}{dI_R} (\because I_L = -I_R)$

At any t,
 $\therefore \frac{d(V_L - V_C)}{dI_L} = -10.$

Hence (B)

4. [Ans .C], $M = xy^2 + \lambda x^2 y$
 $N = (x + y)x^2$
 for exact differential equation

$\frac{\partial M}{\partial y} = \frac{\partial N}{\partial x}$
 $3x^2 + 2xy = 2xy + \lambda x^2$
 $\Rightarrow \lambda = 3$

Option (C) is correct

5. [Ans .C], $\text{Res } f(z) = \lim_{z \rightarrow 1} \frac{d}{dz} [(z - 1)^2 f(z)] = \lim_{z \rightarrow 1} \frac{d}{dz} \left(\frac{50z}{(z+4)} \right) = 8$
 Ans (C)

6. [Ans .B], which leads to very low $f'(x_0)$

7. [Ans .A],

By simple expansion of $e^x = 1 + x + \frac{x^2}{2!} + \frac{x^3}{3!}$, we get the result.

8. [Ans .B], $P = \frac{E^2}{R}$

$\log P = 2 \log E - \log R$

$\frac{\delta P}{P} = 2 \frac{\delta E}{E} - \frac{\delta R}{R}$

$\frac{\delta P}{P} \times 100 = 2 \frac{\delta E}{E} \times 100 - \frac{\delta R}{R} \times 100$


$\frac{\delta P}{P} \times 100 = 2(3) - (-2) = 8$

Ans. (B) is correct

9. [Ans .B],

Correct answer is $\frac{V_0}{V_i} = 1/SCR$

10.

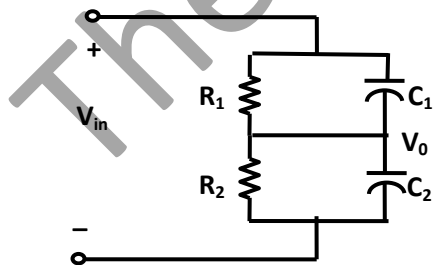

Solution:

$$\frac{V_0}{V_{in}} = \frac{R_2}{R_1 + R_2} - \frac{1 + sC_1R_1}{1 + s \frac{R_1R_2}{R_1 + R_2} (C_1 + C_2)}$$

For $\frac{V_0}{V_{in}} = \text{constant}$,

So, here,

$R_1 C_1 = \frac{R_1 R_2}{R_1 + R_2} (C_1 + C_2)$

$R = 10k$

or $R_1 C_1 = R_2 C_2$

Option (B) is correct

11. [Ans .D]

$\Delta f = k_p A_m = 5k$ B.W. $= 2(fm + \Delta f)$, so when A_m is increased by factor of 3 New
 $\Delta f = 15k$

$$\therefore B.W. = 2(1 + 15) = 32k$$

12. [Ans .B]

13. [Ans .B]

At $T = 300K$, intrinsic concentration $S_i = N_i = 10^{10}$

→ Boron is acceptor impurity

∴ Si is p-type

also Hole concentration $= p \approx N_A = 10^{17}/\text{cm}^3$ and we know that the product of majority and minority carrier is constant.

$$p^n = N:2$$

$$\therefore 10^{17} \times n = 10^{20} \Rightarrow n = 10^3/\text{cm}^3 \text{ (option- B)}$$

14. [Ans .B]

15. [Ans .A]

16. [Ans .B]

17. [Ans .C]

18. [Ans .D], For (D), $y(e^{j\omega}) = e^{j2\omega} \cdot x(e^{j\omega})$

$$|y(e^{j\omega})| = |x(e^{j\omega})|, \forall \omega$$

Hence (D)

19. [Ans .A]

$y[n] = \delta(n) + 2x[n-3]$ is non linear since super position principle fails and time variant as
 $y(n - n_0) \neq T\{x(n - n_0)\}$

20. [Ans .C]

For each amplifier transfer function is $\frac{A}{1 + \frac{s}{\omega_0}}$

Here, $\omega_0 = 2\pi f_0$; f_0 is the 3 dB frequency.

For N identical cascaded stages transfer function is $\frac{A^N}{(1 + \frac{s}{\omega_0})^N}$; dc gain $= A^N$

$$\text{Magnitude of gain} = \frac{A^N}{\left\{1 + \left(\frac{\omega}{\omega_0}\right)^2\right\}^{\frac{N}{2}}}$$

At 3 dB for this cascaded stage,

$$\frac{A^N}{\left\{1 + \left(\frac{\omega}{\omega_0}\right)^2\right\}^{\frac{N}{2}}} = \frac{A^N}{\sqrt{2}}; \text{ which gives}$$

$$\omega = \omega_0 \sqrt{2^{1/N} - 1} \text{ as 3 dB frequency}$$

For 2 stage, $f_{3dB} = f_0 \sqrt{\sqrt{2} - 1} = 0.6436f_0$

21. [Ans .B]

22. [Ans .D]

23. [Ans .B]

24. [Ans .C], In bode – magnitude plot,

Steady state decay $= -20(P - z)$ dB/decade

Given $z = 3$, $\therefore p - z = 3 \Rightarrow p = 6$

Hence (C)

25. [Ans .A]

S^5	1	-1	-4
S^4	-1	-7	-4
S^3	-8	-8	
S^2	-6	-4	
S^1	-8/3		
S^0	-4		

number of sign changes = number of roots with positive real part = 1


\therefore number of roots on left half of s – plane = 5-1 = 4

Hence (A)

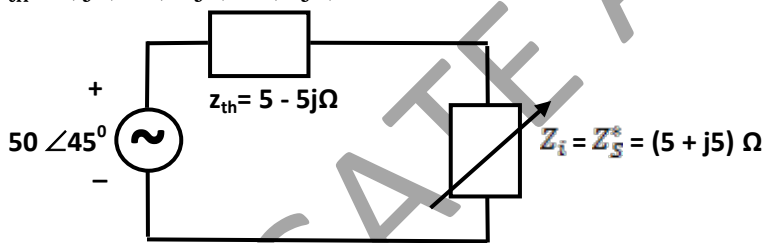26. [Ans .A]

$$V_{th} = \left(\frac{50 \angle 0^\circ}{-j5 + j5 + 5} \right) (j5 + 5\Omega) = 10 \angle 0^\circ \cdot 5\sqrt{2} \angle 45^\circ = 50\sqrt{2} \angle 45^\circ$$

$$Z_{th} = (-j5) \parallel (5 + j5) = (5 - j5) \Omega$$



$$I = \frac{50\sqrt{2} \angle 45^\circ}{5 - j5 + 5 + j5} = 5\sqrt{2} \angle 45^\circ$$

$$P_{max} = |I|^2 (5) = 125w.$$

Ans (A)

27. [Ans .B], $A = \begin{bmatrix} -1 & 2 & 3 \\ 0 & 4 & -1 \\ 0 & 0 & 1 \end{bmatrix}$

Eigen value of A are $\lambda_1 = -1, \lambda_2 = +1, \lambda_3 = 4,$

Eigen value of matrix $B = \lambda^3 + \lambda^2 + A + I,$ are

$$[\lambda_1]_B = \lambda_1^3 + \lambda_1^2 + \lambda_1 + 1 = 0$$

$$[\lambda_2]_B = \lambda_2^3 + \lambda_2^2 + \lambda_2 + 1 = 4$$

$$[\lambda_3]_B = \lambda_3^3 + \lambda_3^2 + \lambda_3 + 1 = 85$$

$$\text{Trace of } B = [\lambda_1]_B + [\lambda_2]_B + [\lambda_3]_B = 89$$

Option (B) is correct

28. [Ans .B], $(D^2 - 2D + 1)y = \frac{e^x}{x}$

$$C.F = (C_1 + C_2x) e^x$$

$$P.I = \frac{1}{(D-1)^2} \frac{e^x}{x} = e^x \cdot \frac{1}{(D+1-1)^2} \cdot \frac{1}{x}$$

$$= e^x \frac{1}{D} \log x = e^x \int \log x \, dx$$

$$= e^x(x \log x - x)$$

$$\text{complete solution} = (C_1 + C_2x) e^x + e^x(x \log x - x)$$

$$= (C_1 + C_2x + x \log x - x) e^x$$

Option (B) is correct

29. [Ans .C], Probability of drawing a green balls from box y if the transferred ball is green ,


$$P_1 = \frac{4}{6} \times \frac{8}{13} = \frac{16}{39}$$

probability of drawing of green ball from box y if the transferred ball is red , $P_2 = \frac{2}{6} \times \frac{7}{13} = \frac{7}{39}$

$$\text{Required probability} = P_1 + P_2 = \frac{22}{39}$$

Option (C) is correct

30.

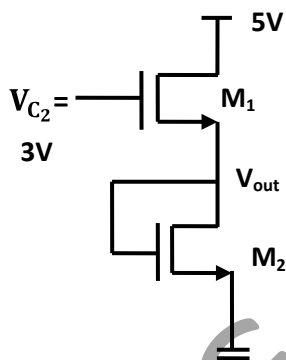

M_2 is diode connected so is in saturation

For M_1 : $V_D = 5V$ & $V_G = 3V$

$V_{Th} = 1V$ (given) \rightarrow Threshold voltage

So, $V_D > V_G - V_{Th}$; so M_1 is also in saturation


Now applying KCL at V_{out} ;

$$I_{M_1} = \mu_w C_{ox} \left(\frac{W}{L}\right) (V_G - V_{out} - V_{Th})^2 = I_{M_2} = \mu_w C_{ox} \left(\frac{W}{L}\right) (V_{out} - V_{Th})^2$$

$$I_{M_1} = I_{M_2} \text{ gives, } V_{out} = \frac{V_G}{2} = 1.5V$$

Option (C)

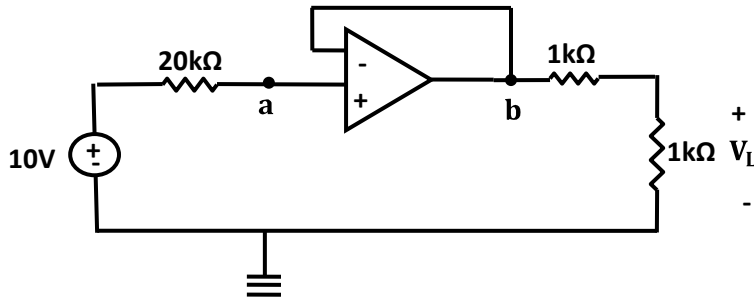31. [Ans .C], Applying Thevenin's equivalent to left side of (A) point



$$v_a = 10V; \quad v_b = 10V \text{ (buffer)}$$

$$V_L = v_b \cdot \frac{1k\Omega}{1k\Omega + 1k\Omega} = 5V$$

Option (C)

32. [Ans .C]

Solution: For given system,

$$\Phi(S) = (SI - A)^{-1} = \frac{1}{(S^2 + 2)} \begin{bmatrix} S & 1 \\ -2 & S \end{bmatrix}$$

$$\Phi(t) = L^{-1}(\Phi(S)) = \begin{bmatrix} \cos \sqrt{2}t & 1/\sqrt{2} \sin 2t \\ -\sqrt{2} \sin \sqrt{2}t & \cos \sqrt{2}t \end{bmatrix}$$

$$|\Phi(t)| = 1 = \lambda_1 \cdot \lambda_2$$

$$\text{Given } \lambda_1 = \lambda, \therefore \lambda_2 = 1/\lambda$$

Hence (C)

33. [Ans .A]

$$R_{XY}(t_1, t_0) = 1.5\delta(t_1 - t_0 + \tau) + 1.5\delta(t_0 - t_1 + \tau)$$

34. [Ans .A]

35. [Ans .D]

36. [Ans .C]

$$V_{bi} = \frac{KT}{9} \ln \left(\frac{N_A N_D}{N_i^2} \right) = 0.026V \ln \left(\frac{5 \times 10^{16} \times 10^{16}}{10^{20}} \right) = 0.76 \text{ V}$$

$$W_d = \left[2 \frac{\epsilon_{si}}{q} V_{bi} \left(\frac{1}{N_A} + \frac{1}{N_D} \right) \right]^{\frac{1}{2}}$$

$$= \left[2 \times \frac{10^{-12}}{1.6 \times 10^{-19}} \times 0.76 \times \left(\frac{1}{5 \times 10^{16}} + \frac{1}{10^{16}} \right) \right]^{\frac{1}{2}}$$

$$= 0.346 \mu\text{m}$$

$$\therefore V_{bi} = 0.76 \text{ V}, W_d = 0.346 \mu\text{m}$$

37. [Ans .D]

38. [Ans .B]

39. [Ans .D]

40. [Ans .C]

The energy of $y(t) = 3x(t) \cdot e^{-j3t}$ is,

$$\begin{aligned}
 E_x &= \frac{1}{2\pi} \int_{-\infty}^{\infty} |X(\omega)|^2 d\omega \\
 E_y &= \frac{1}{2\pi} \int_{-\infty}^{\infty} |Y(\omega)|^2 d\omega \\
 &= \frac{1}{2\pi} \int_{-\infty}^{\infty} 9|X(\omega)|^2 d\omega \\
 &= \frac{9}{2\pi} [2(\omega_0 - \omega_1) \times 16 + 2 \times (\omega_1) \times 9] \\
 &= \frac{9}{2\pi} [32\omega_0 - 32\omega_1 + 18\omega_1] \\
 &= \frac{9[32\omega_0 - 14\omega_1]}{2\pi} \\
 &= \frac{9(16\omega_0 - 7\omega_1)}{\pi}
 \end{aligned}$$

41. [Ans .D]

For $2^n \mu(n)$, Z.T. is $|z| > 2$

For $-\left(\frac{1}{3}\right)^n \mu(-n-1)$, Z.T. is $|z| < 1/3$.

Intersection of ROCs is \emptyset .

Hence (D)

42. [Ans .B]

$$y[n] = A x[n-n_0] = A \sin[\omega_0(n - n_0) + \phi]$$

The group delay function,

$$\frac{-d\theta(\omega)}{d\omega} = \text{tg} = n_0 \text{ here}$$

$$\text{So, } d\theta(\omega) = -n_0 d\omega/\omega = \omega_0$$

$$\therefore \theta(\omega) = -n_0\omega_0 + k^1$$

To avoid phase change $k^1 = 2\pi k$

This form of $\theta(\omega)$ is called as unwrapped phase.

43. [Ans .A]

First we need to calculate the mobility of electron (μ_e) we know that drift velocity of hole is given by,

$$V_{\text{drift}} = \mu_p E = \mu_p \frac{V_{\text{drift}}}{E} = \frac{3 \times 10^5 \text{ cm/sec}}{1000 \text{ v/cm}} = 300 \text{ cm}^2/\text{v.sec}$$

$$\mu_e = 2 \times \mu_p = 600 \text{ cm}^2/\text{v.sec}$$

$$\text{Resistivity is given by, } \rho = \frac{1}{q\mu_n n + q\mu_p p} \approx \frac{1}{q\mu_n n} \text{ (since } n \gg p \text{)}$$

$$\therefore \rho = \frac{1}{1.602 \times 10^{-14} \times 600 \times 10^{17}} = 0.104 \Omega \text{ cm}$$


44. [Ans .C]

T = Time period

Average value

$$= \frac{1}{T} [\text{Area of Trapezoid}] = \frac{1}{T} \times \left[\frac{1}{2} \times \left(\frac{T}{2} + \frac{T}{4} \right) \times 10 \right]$$

$$= 3.75 \text{ V}$$

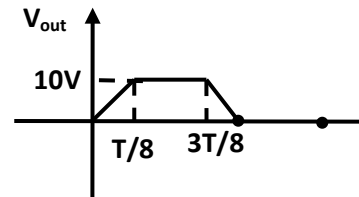

45. [Ans .B]

$$\begin{aligned}
 E &= I_m (E_s e^{j\omega t}) \\
 \rightarrow E_s &= 20e^{j\beta z} a_y, \text{ where } \omega = 10^8 \text{ ----- (1)} \\
 \nabla \cdot E_s &= \frac{\partial E_{ys}}{\partial y} = 0 \\
 \nabla \times E_s &= -j\omega\mu H_s \rightarrow H_s = \frac{\nabla \times E_s}{-j\omega\mu} \\
 &= \frac{1}{-j\omega\mu} \left[-\frac{\partial E_{ys}}{\partial z} a_x \right] = -\frac{20\beta}{\omega\mu} e^{-j\beta z} a_x \\
 \nabla \times H_s &= j\omega t E_s \rightarrow E_s = \frac{\nabla \times H_s}{j\omega t} \\
 &= \frac{1}{j\omega\mu} \left(\frac{\partial H_{xs}}{\partial z} \right) a_y = \frac{20\beta^2 e^{-j\beta z}}{\omega^2\mu\epsilon} a_y \text{ ----- (2)}
 \end{aligned}$$

Comparing (1) and (2)

$$20 = \frac{20\beta^2}{\omega^2\mu\epsilon} \Rightarrow \beta = \pm \omega\sqrt{\mu\epsilon} = \pm 1/3$$

46. [Ans .B]

Solution: $\beta_1 = \frac{\omega}{c} = \frac{1}{3}$, $n_1 = n_0 = 120\pi \rightarrow$ for free space

$\beta_2 = \omega\sqrt{\mu\epsilon} = \frac{4}{3}$, $n_2 = 2n_0 \rightarrow$ for lossless dielectric

Given: $H_i = 10\cos(10^8t - \beta_1 z)a_x$

$$\Rightarrow E_{i0} = 10 n_0$$

So $E_i = -10n_0 \cos(10^8t - \beta_1 z) a_x \text{ mv/m}$

$$\Gamma = \frac{n_2 - n_1}{n_2 + n_1} = \frac{1}{3} = \frac{E_i}{E_r} \Rightarrow E_r = \frac{E_i}{3}$$

$E_r = -\frac{40}{3} n_0 \cos(10^8t - \frac{4}{3}z) a_y \text{ mv/m}$

$H_r = \frac{20}{3} \cos(10^8t - \frac{4}{3}z) a_x \text{ mA/m}$

47. [Ans .A]

For A, poles are root of $s^2 + 5s - 6 = 0$

\therefore Poles are -6 & +1

\therefore A is unstable

$$\text{For B, } T(s) = \frac{4}{1 + \frac{4}{(s^2+5s-6)} \cdot \frac{(s-1)}{(2)}} = \frac{4}{(s^2+7s-8)}$$

\therefore Poles are roots of $s^2 + 7s - 8 = 0$

\therefore Poles are -8 & +1

\therefore B is unstable

Hence (A)

48. [Ans .B], $i_L(0) = 2A$, $V_C(0) = 2V$

$$i_L(t) = 2e^{-t}$$

$$\frac{di_L(t)}{dt} = -2e^{-t}, \text{ At } t = 0^+ \quad \frac{di_L(t)}{dt} \Big|_{t=0^+} = -2 \text{ A/S}$$

Option (B)

49. [Ans .C], $\frac{dV_C}{dt} \Big|_{t=0^+} = -2 \text{ V/sec}$, $\frac{dI_L}{dt} \Big|_{t=0^+} = -2 \text{ A/sec}$

$$\frac{dV_C}{dI_L} = 1$$

Hence (C)

50. [Ans .D]

The number of bits in the PCM system are,

$$n = 7 \text{ bits}$$

$$\left(\frac{S}{n}\right)_{\text{dB}} = 1.8 + 6n \text{ dB}$$

$$= 43.8 \text{ dB.}$$

51. [Ans .C]

Signaling rate is given by

$$\gamma = \vartheta f_s$$

$$r = 56 \times 10^3 \text{ and}$$

$$\vartheta = 7 \text{ bits}$$

$$f_s = 8 \times 10^3 \text{ Hz}$$

$$f_s \geq 2 f_m$$

$$\therefore f_m \leq 4 \text{ KHz}$$

52. [Ans .C], Feed back factor $\beta = \frac{R_1}{R_1 + R_2}$

Option (C)

53. [Ans .C], If open loop given $= A = 10^4$

$$A_f = \text{closed loop given} = \frac{A}{1 + A\beta}$$

$$\text{Now, } A_f = 10 = \frac{A}{1 + A\beta}; \beta = \frac{\frac{A}{10} - 1}{A}$$

$$\beta = \frac{R_1}{R_1 + R_2} = \frac{1}{1 + \frac{R_2}{R_1}} = \frac{10^3 - 1}{10^4} = \frac{999}{10^4}$$

$$\text{so, } 1 + \frac{R_2}{R_1} = \frac{1}{999/10^4} = \frac{10^4}{999}$$

$$\text{so, } \frac{R_2}{R_1} = \frac{10^4}{999} - 1 = \frac{9001}{999} \approx 9.01$$

Option (C)

54. [Ans .B]

Solution: $N = z^+ - p^+$

$$N = -2, z^+ = 0, \therefore p^+ = 2$$

Type of system = 2, \therefore order = $2 + p^+ = 4$

Hence (B)


55. [Ans .B], root locus branches = $|2 - P| = 4$

type of system is 2 \Rightarrow 2nd order pole at 0
root locus starts from open loop poles.

Hence from 0

\therefore Hence (B)

56. [Ans. D]

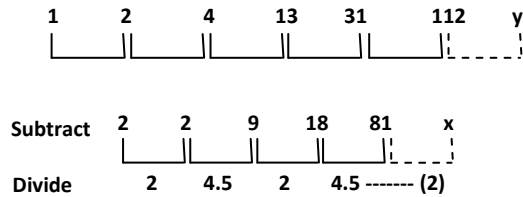

$$81 \times 2 = x$$

$$112 + 81 \times 2 = y = 274$$

57. [Ans. A]

As the fruit seller is buying equal lots, we will have to make number of oranges of both the lots equal. Also, since he is selling all the orange, we will have to make the number of oranges brought and sold equal.

$$\therefore \text{L.C.M of } 5, 4, 9 = 180.$$

The fruit seller is buying two lots of oranges, each lot having 180 oranges.

$$\therefore 1^{\text{st}} \text{ lot} = 36 \text{ Rs.} \quad \Rightarrow \text{Total spent} = 45 + 36 = 81 \text{ Rs.}$$

$$2^{\text{nd}} \text{ lot} = 45 \text{ Rs.}$$

The fruit seller sells 9 oranges for 2 Rs. Therefore 560 Oranges for 80 Rs.

$$\therefore \text{Loss of 1 Rupee as loss \%} = \frac{1}{81} \times 100 = 1.23\%.$$

58. [Ans. C]

59. [Ans. A]

60. [Ans. B]

Choices A & C do not state the comparison logically. The expression *as old as* indicates equality of age, but the sentence indicates that the Brittany monuments predate the Mediterranean monuments by 2,000 years.

In B, the best choice, *older than* makes this point of comparison clear. B also correctly uses the adjective

61. [Ans. C]

62. [Ans. B]

63. [Ans. B]

In one day X can finish $1/15^{\text{th}}$ of the work

In one days Y can finish $1/10^{\text{th}}$ of the work.

Let us say that in one day Z can finish $1/2^{\text{th}}$ of the work.

When all the three work together in one day they can finish $\frac{1}{15} + \frac{1}{10} + \frac{1}{2} = \frac{1}{5}$ of the work

$$\therefore \frac{1}{2} = \frac{1}{30}$$

$$\therefore \text{Ratio of efficiencies} = \frac{1}{5} : \frac{1}{10} : \frac{1}{30} = 2 : 3 : 1.$$

\therefore Z receives $1/6^{\text{th}}$ of the total money.

\therefore Accordingly money is divided as 240: 360 : 120.

$$\Rightarrow Z = 120$$

64. [Ans. D]

The probability that a customer entered the store makes a purchase = 0.4.

$$\Rightarrow 2 \text{ customers make a purchase and one does not is } (0.4)^2 \times 0.6$$

The two of the three people can be selected in 3C_2 or 3 ways.

$$\therefore \text{Required probability} = 3 \times 0.4^2 \times 0.6 = 0.288.$$

65. [Ans. C]

$$\left. \begin{array}{l} E_1, E_2, E_3 \rightarrow \text{English men} \\ F_1, F_2, F_3 \rightarrow \text{French men} \end{array} \right\} \begin{array}{l} 1. E_1 \leftrightarrow E_2 \\ E_2 \leftrightarrow E_3 \\ F_1 \leftrightarrow F_2 \\ F_2 \leftrightarrow F_3 \\ F_3 \leftrightarrow E_3 \\ E_3 \leftrightarrow E_2 \\ E_2 \leftrightarrow E_1 \\ F_3 \leftrightarrow F_2 \\ F_1 \leftrightarrow F_1 \end{array} \left. \vphantom{\begin{array}{l} E_1, E_2, E_3 \\ F_1, F_2, F_3 \end{array}} \right\} 9 \text{ calls}$$